


NWEN 242

5. Arithmetic and logic unit (ALU)




Designing a circuit to do 1-bit addition

- A single-bit addition

 

| A | b | CarryIn | CarryOut | Sum |
|---|---|---------|----------|-----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

 

So how do we do subtraction?


- Remember we do not actually subtract

$$A - B$$

- Instead, we perform the following two steps
 - Calculate the **two's complement** of the negative number (**-B**)
 - Add **A** and **-B** through normal addition




1-bit ALU with subtraction

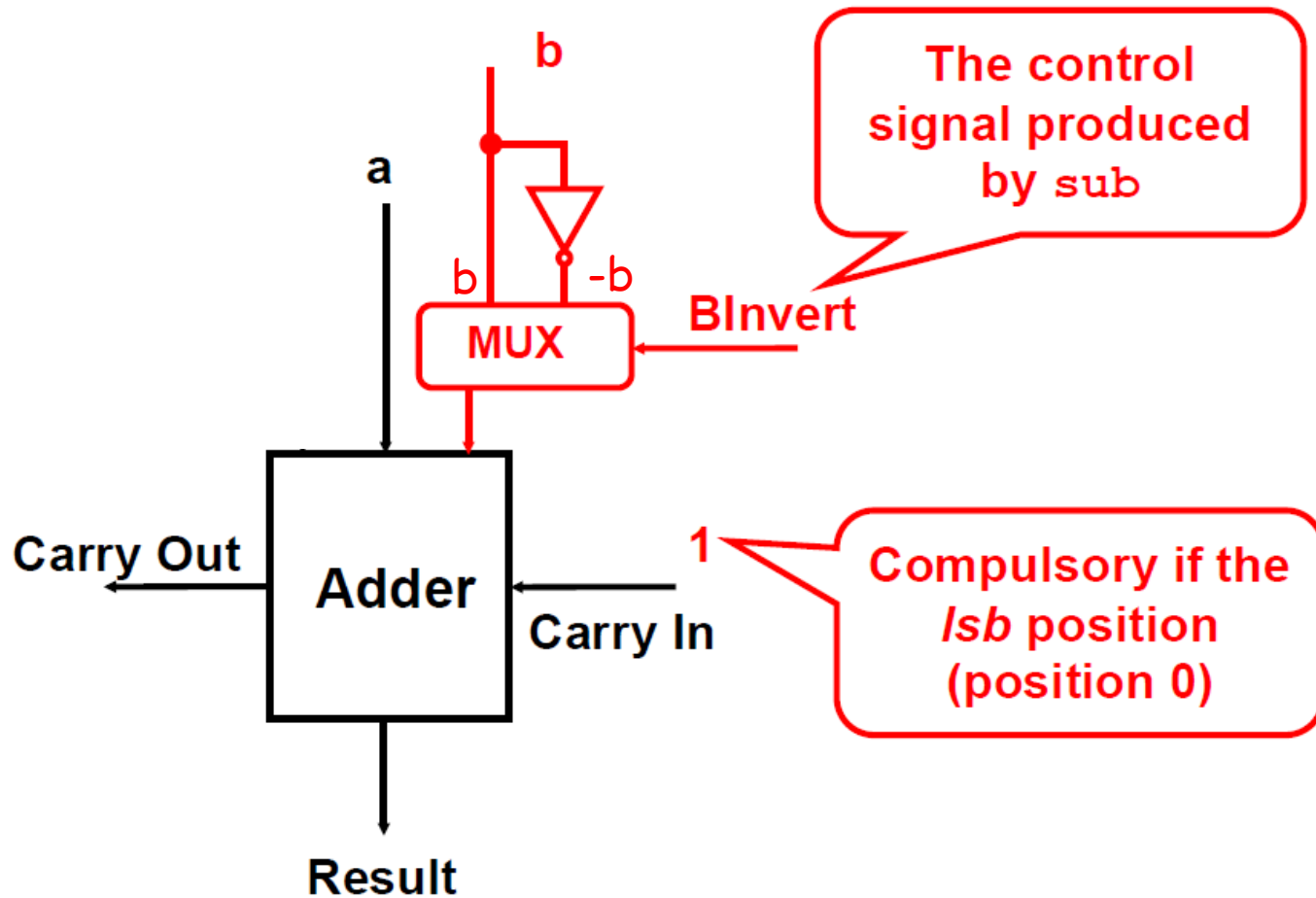

Circuit for a 1-bit ALU




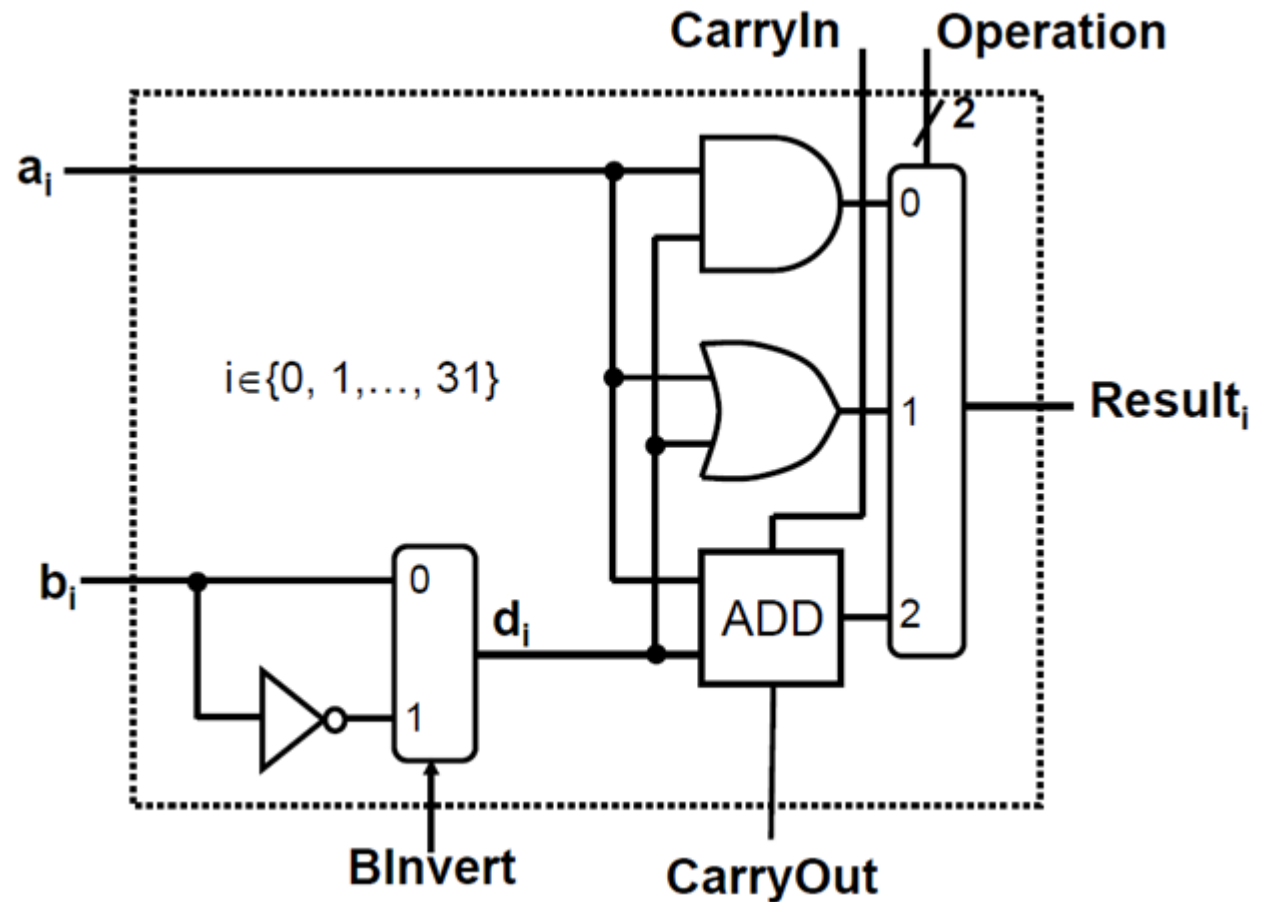- Notice that the operations are always performed but we don't care about the output




Quick exercise

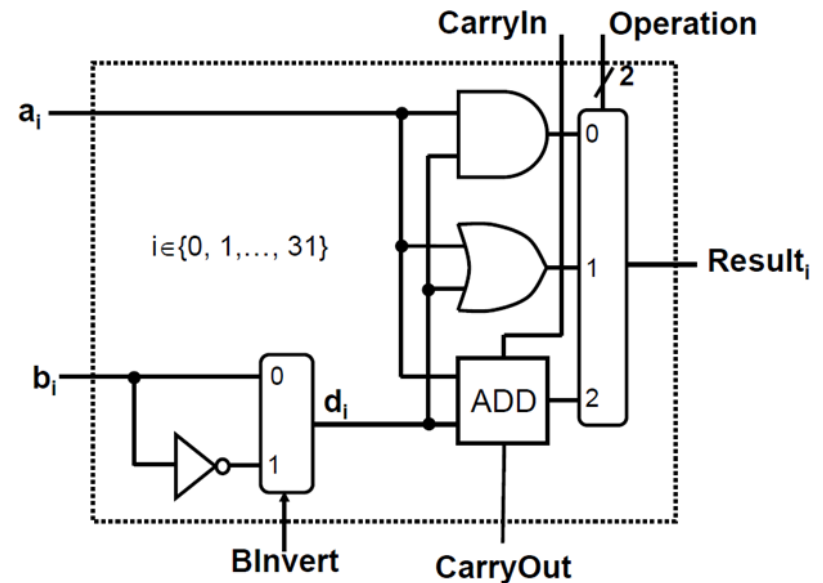- What would be the suitable control input in order to perform an **AND** operation?
 - A. BInvert = 1, Operation = 01
 - B. BInvert = 0, Operation = 01
 - C. BInvert = 1, Operation = 10
 - D. BInvert = 0, Operation = 00



32-bit (Ripple Carry) ALU

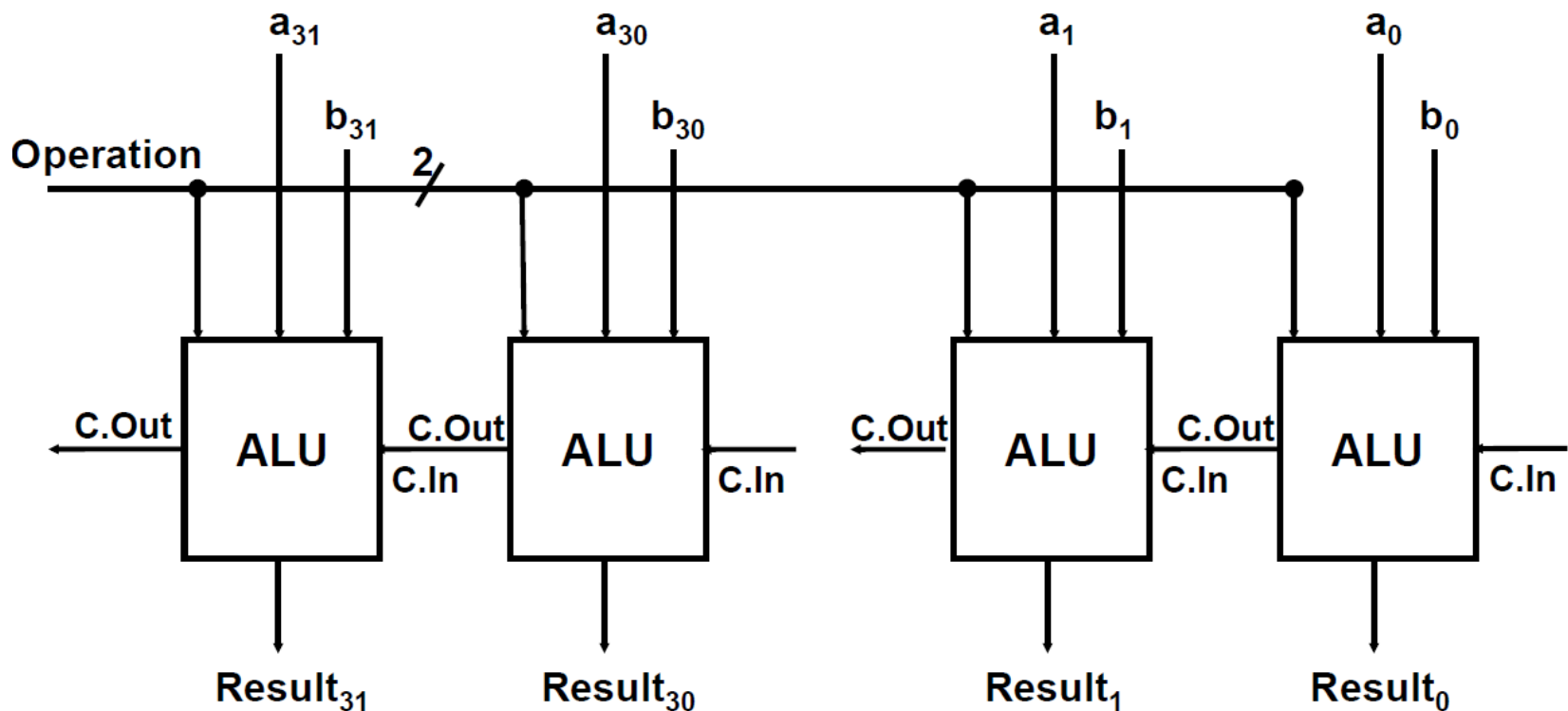- Does ADD, SUB, OR and AND on 32-bits operands a and b
- Produces answer as **Result** and **CarryOut**






Extending ALU to do slt

- Consider the following `slt` instruction:

`slt $d, $s, $t`


- Set `$d` to **1** if `$s < $t`, otherwise set `$d` to **0**
- Note
 - If `$s < $t`, then `$s - $t` is negative and **bit 31** of the result is **1**
 - If `$s ≥ $t`, the **bit 31** of the result is **0**
- Set comparison result
 - Copy the **sign bit** of the result `$s - $t` to bit **0** of `$d`
 - Other bits of `$d` are simply set to **0**

Circuit for producing comparison result

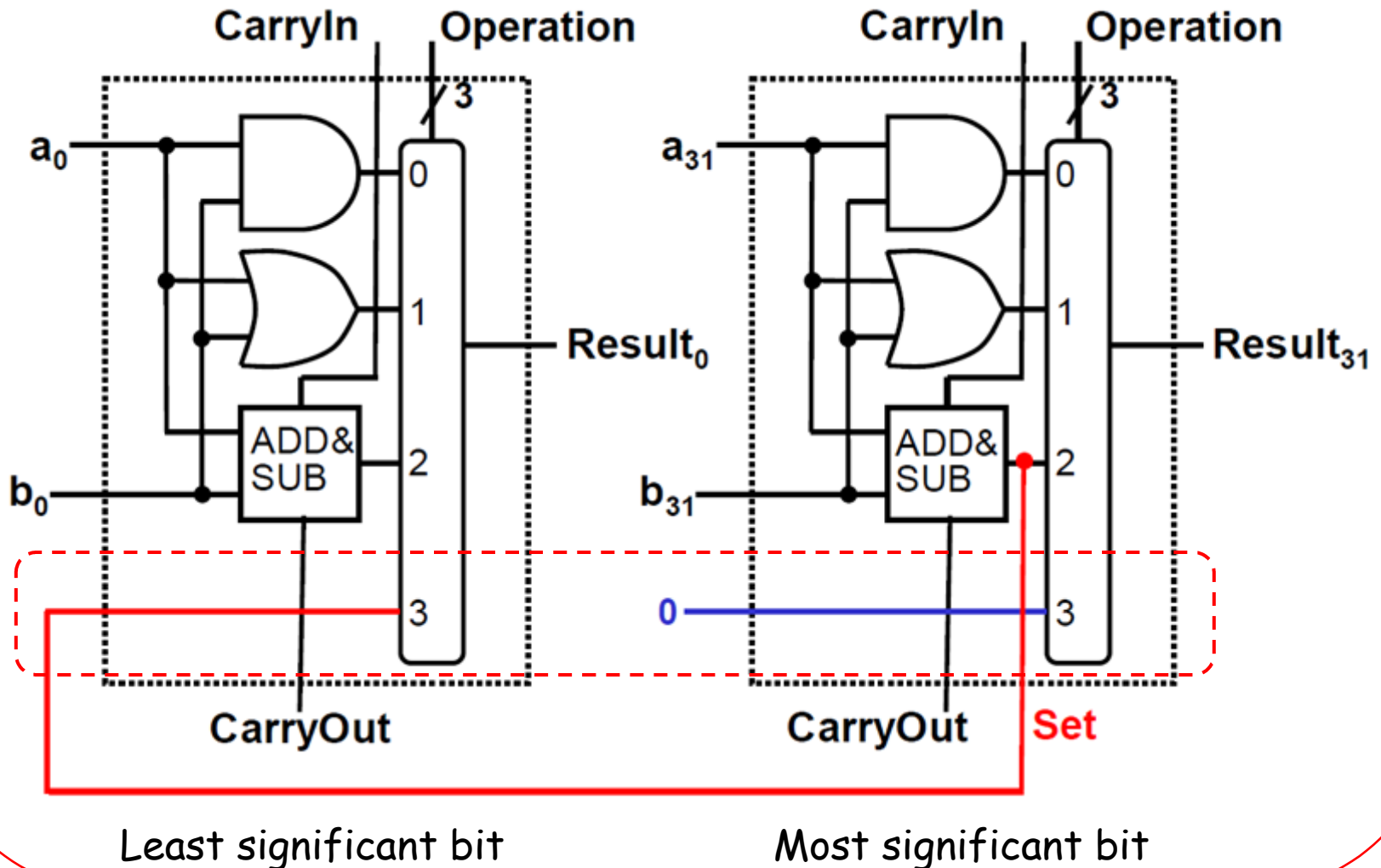

32-bit ALU with slt

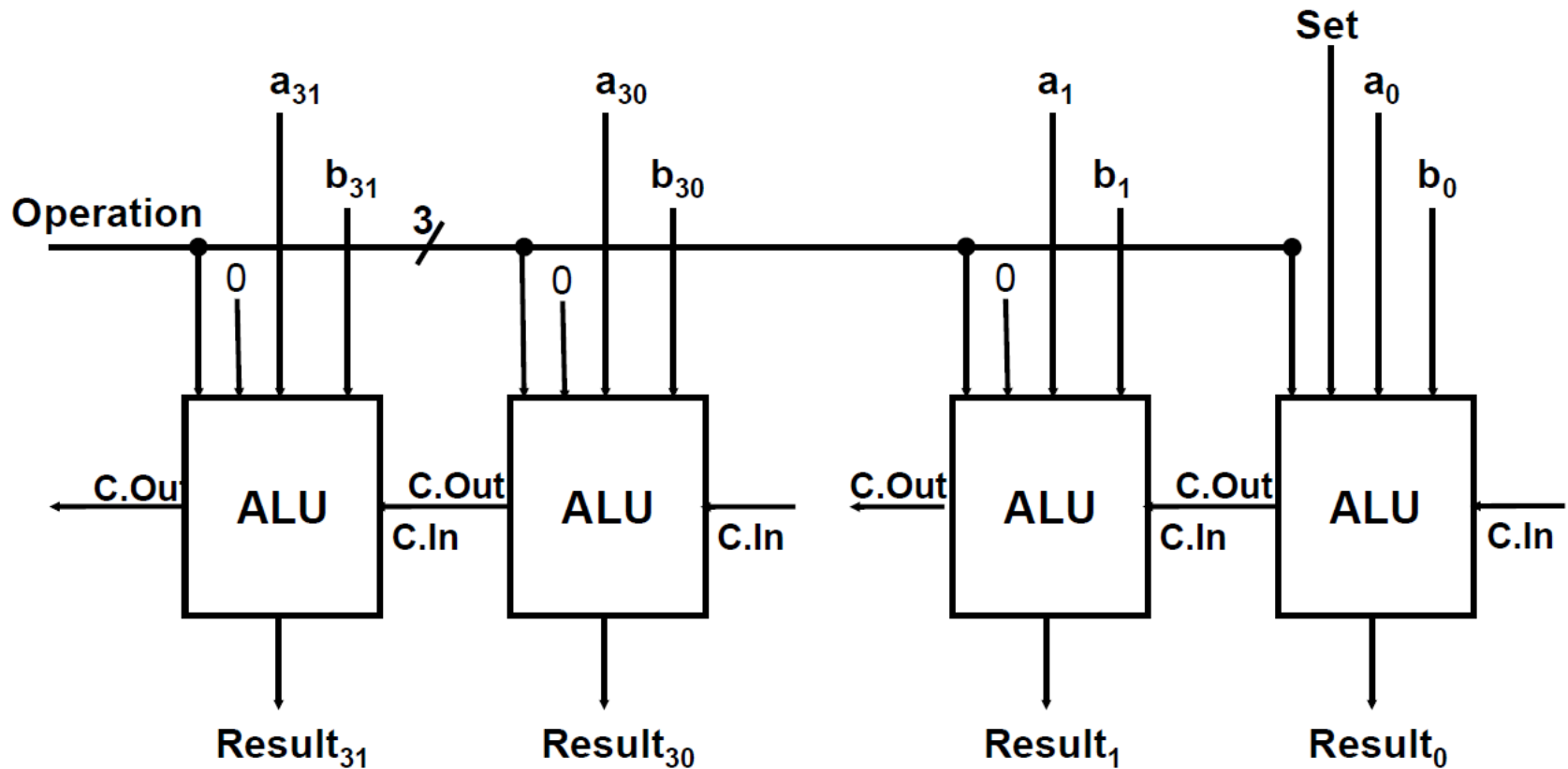- Supports ADD, SUB, OR, AND, and SLT on 32-bit operands a and b



Implementing beq




- Consider the branch on equal instruction

`beq $s, $t, label`

- We need a control signal, called **zero**


- Procedure

 - Use ALU to subtract t from s
- OR the result bits
- Invert



Block representation of ALU

 - From now on, we shall refer to ALU using the following graphical symbol:



Overflow detection


| Operation | A Operand | B Operand | Result | Overflow |
|-----------|------------|------------|------------------------|----------|
| add | $A \geq 0$ | $B \geq 0$ | $\text{Result} < 0$ | Yes |
| add | $A < 0$ | $B < 0$ | $\text{Result} \geq 0$ | Yes |
| sub | $A \geq 0$ | $B < 0$ | $\text{Result} < 0$ | Yes |
| sub | $A < 0$ | $B \geq 0$ | $\text{Result} \geq 0$ | Yes |

- Bit-level relationship (the most significant bit)
 - d is the two's complement of b

| BInvert | a_{31} | d_{31} | sum_{31} | Overflow |
|---------|----------|----------|-------------------|----------|
| 0 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 |

$$\overline{a_{31}} \cdot \overline{d_{31}} \cdot \text{sum}_{31} + a_{31} \cdot \overline{d_{31}} \cdot \overline{\text{sum}_{31}}$$

Overflow detection hardware

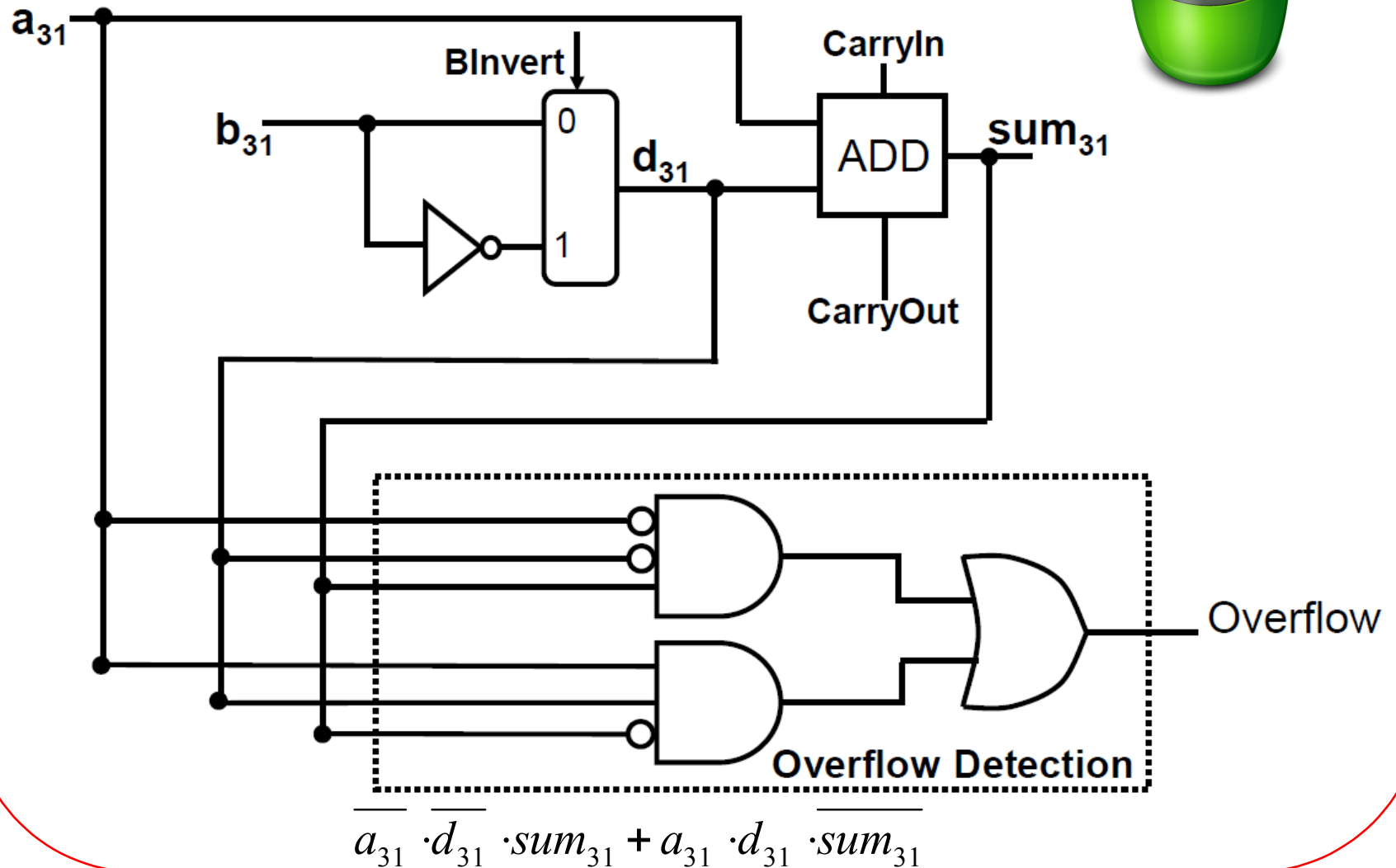

Quick exercise

- Will overflow affect the ALU comparison result?
 - A. Yes
 - B. No
- Will overflow affect the zero output?
 - A. Yes
 - B. No

Summary

- A 1-bit ALU always performs
 - AND, OR
 - Either a 1-bit add or a 1-bit subtract
 - SLT
- A multiplexor decides what will appear at the output according to the **operation on selector inputs**
- A 32-bit ALU performs arithmetic and logic operations on whole words
- Instructions slt and beq use ALU to **subtract target (rt) register from source (rs) register**

