

## NWEN 242

### 6. Processor: single cycle datapath



## Agenda



- What is a processor datapath?
- Design instruction-fetch logic
- Design 3 mini-datapaths
  - **R-type** (for e.g. add)
  - **Memory** (for e.g. lw and sw)
  - **Branch** (for e.g. beq)
- Combine the instruction-fetch logic with the 3 mini-datapaths

## What is a processor datapath?




- Datapath
  - Literally, the path along which data flows
  - Hardware that connects:
    - Instruction memory
    - Register file
    - ALU
    - Data memory


 
## Quick exercise

- If a processor operates on **1 GHz**, the duration of 1 clock cycle is
  - A. 1 nanosecond
  - B. 1 second
  - C. 1 minute
  - D. None of the above



## Quick exercise




- The relationship between **1 nanosecond** and **1 second** is approximately the same as between:
  - A. 1 second and 1 day
  - B. 1 second and 16 weeks
  - C. 1 second and 12 months
  - D. 1 second and 32 years

## Answer

- 1 second =  $10^9$  nanoseconds, therefore 1,000,000,000 ns
- 1 day =  $24 \times 3600 = 86,400$  seconds
- 16 weeks =  $16 \times 7 \times 86,400 = 9,676,800$  seconds
- 12 months =  $365 \times 86,400 = 31,536,000$  seconds
- 32 years =  $32 \times 31,536,000 = 1,009,152,000$  seconds

 
## How instructions are fetched

- Instruction memory holds program instructions
- **PC** (program counter) holds the address of the instruction to be executed next
- Every clock cycle a new instruction is fetched from the memory and PC is incremented by a **4 adder**



## R-type mini datapath: what's required


 
- Example instructions
  - add \$1, \$2, \$3      ➡    add \$1, \$1, \$3 ?
  - sub \$20, \$2, \$30
  - slt \$1, \$16, \$17
- General requirement
  - Two **source** registers
  - An **ALU** operation
  - One **destination** register






## Where the instruction bits come from?

- Example

  


## Implement R-type mini datapath

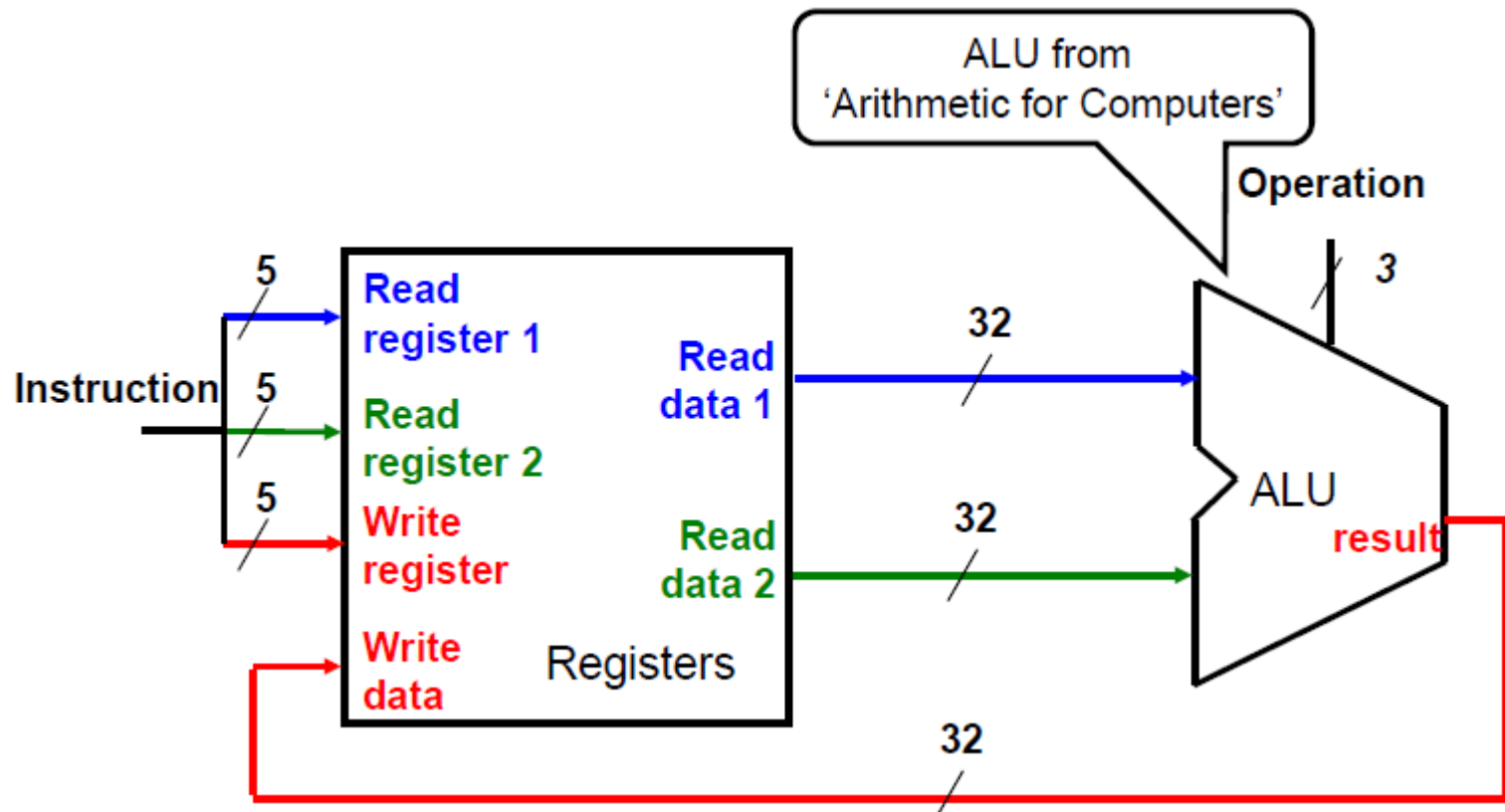
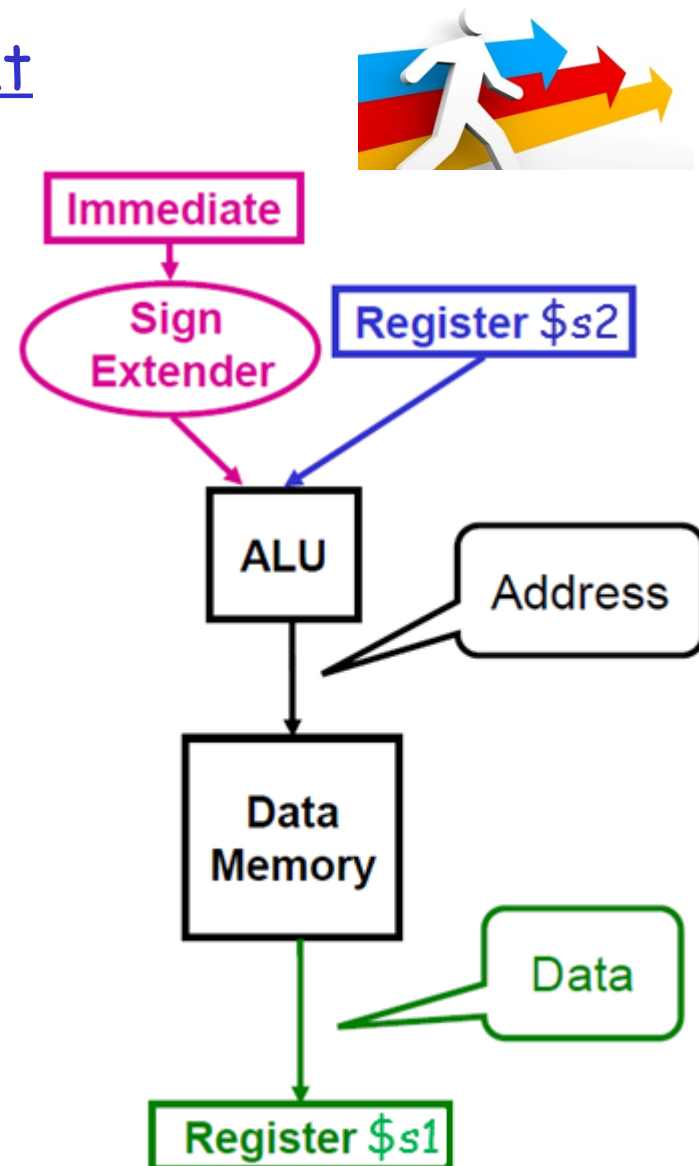
## Read from memory: I-format


- Typical instruction:
  - lw **\$s1**, **offset**(\$s2)
- Required activities
  - Read of the base address register
    - rs=\$s2
  - **16-to-32** bit sign extension for the immediate field (i.e. **offset**)
  - ALU add to calculate memory address
  - Access data memory to read a word at the calculated address
  - Write data to the destination register
    - rt=\$s1


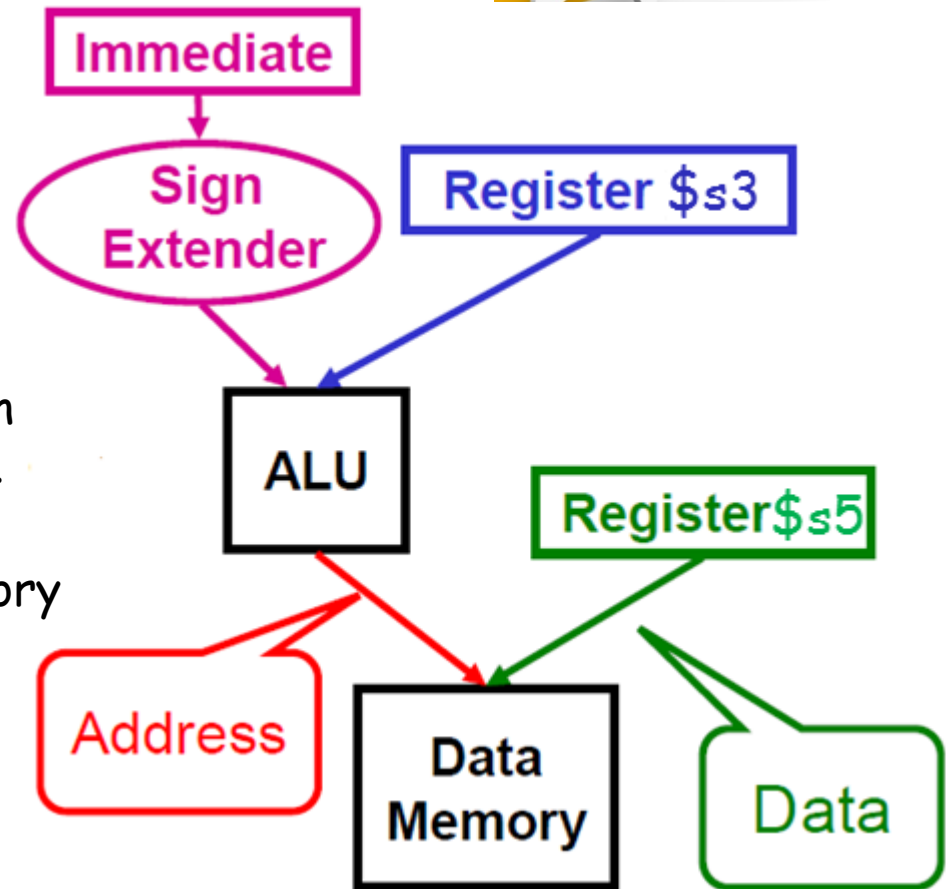
## Write to memory: what's required




- Typical instruction
  - `sw $s5, offset($s3)`
- Required activities
  - Read of the base address register
    - `rs=$s3`
  - 16-to-32 bit sign extension of the immediate field (i.e. `offset`)
  - ALU add to calculate memory address
  - Read data from register
    - `rt=$s5`
  - Store a word from `$s5` to data memory




## Quick exercise

- If **sign extension** and **register reading** can be performed in **1ns**
- If **ALU** takes **1ns**
- If **accessing the memory** needs to be performed in **2ns**
- If **writing a register** needs to be performed in **1ns**
- What is the total time required for **lw** and **sw**?
  - A. lw=5ns, sw=5ns
  - B. lw=5ns, sw=4ns
  - C. lw=4ns, sw=5ns
  - D. None of the above
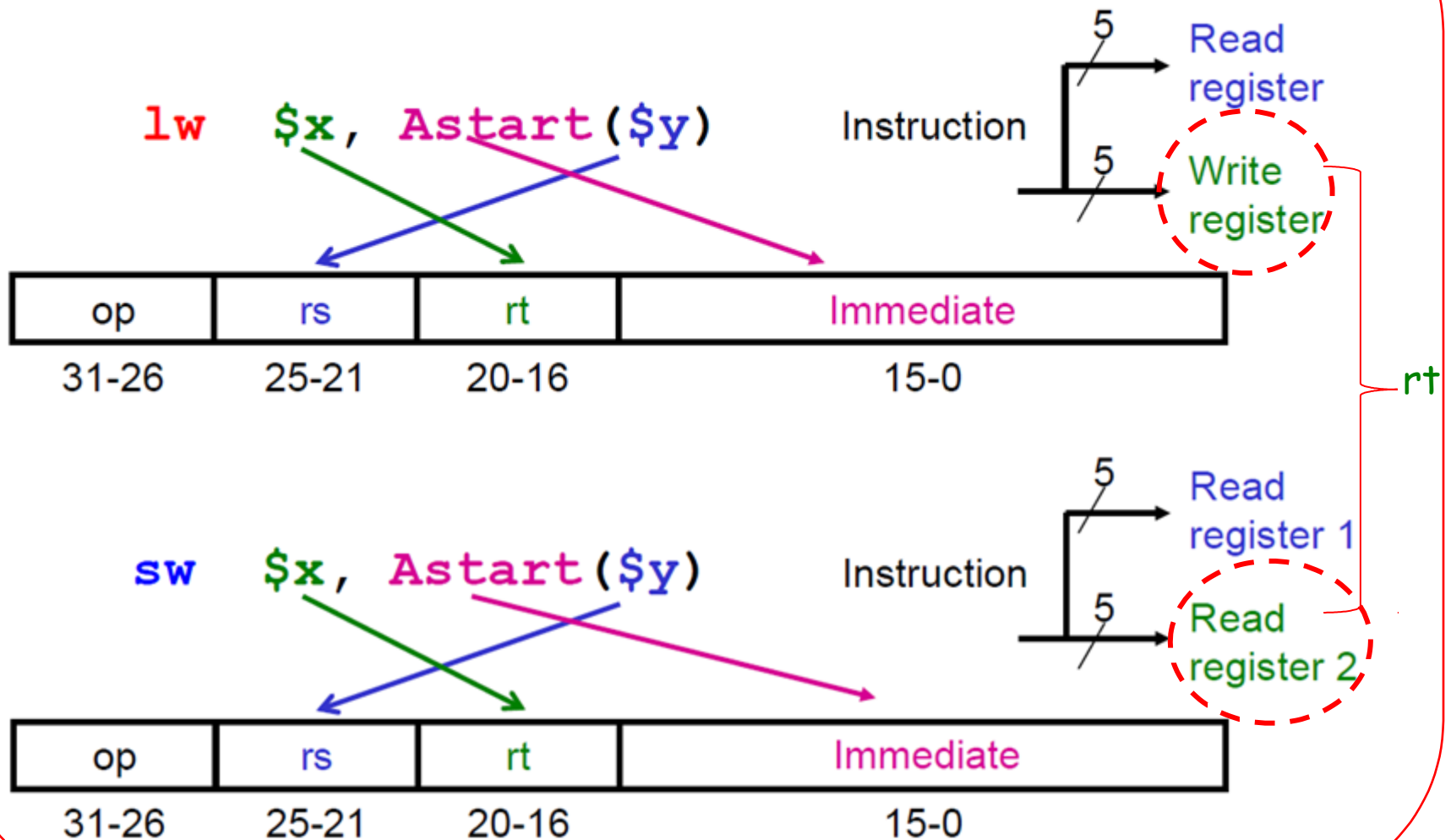
## Where do the instruction bits come from?




## Implement memory mini datapath

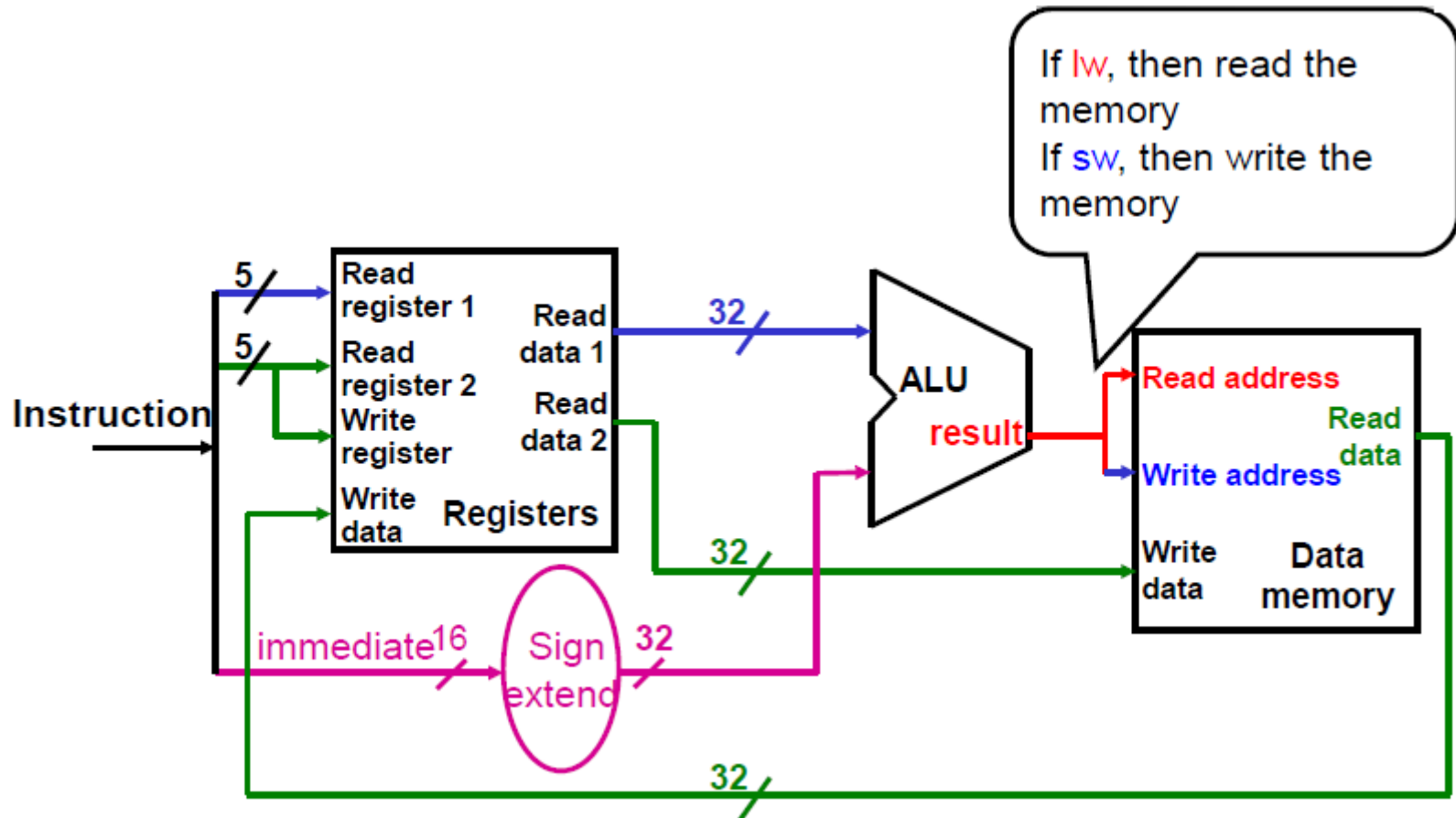

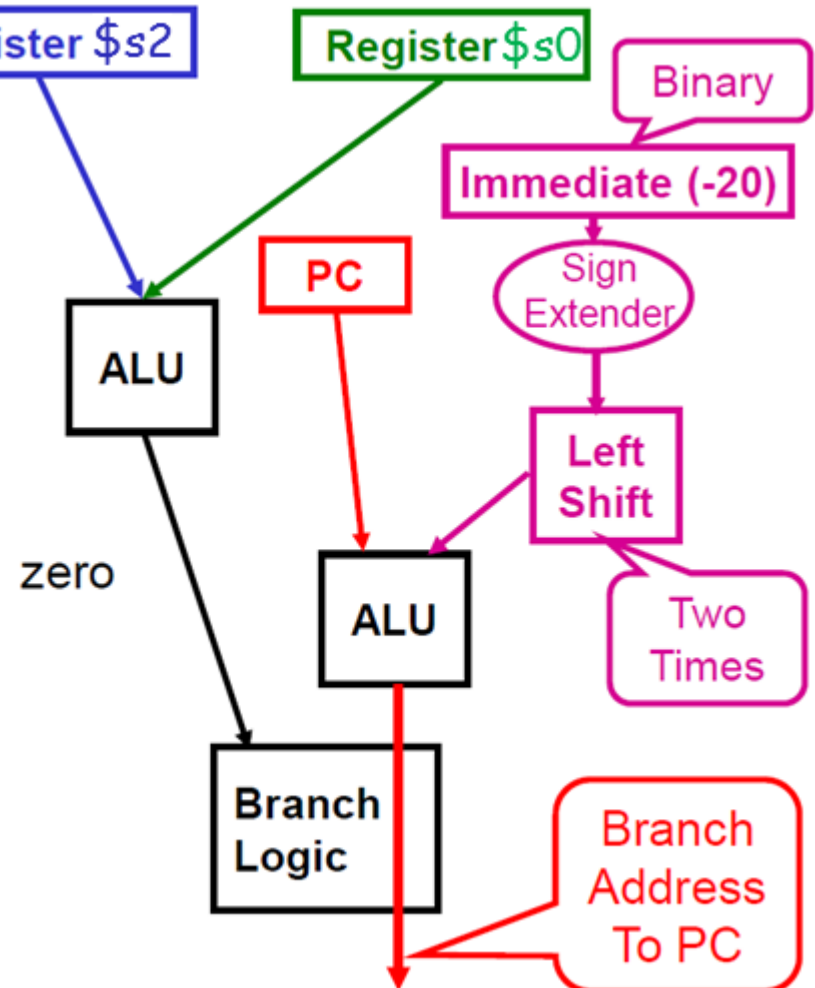
## Branch mini datapath: what's required

- Typical instruction
  - beq \$s2, \$s0, -20
- Required activities
  - Read two register
    - \$s2, \$s0
  - ALU compare operation
  - 16-to-32 bit sign extension
  - Left shift to convert word into byte offset
  - ALU add to calculate branch address from PC and offset
  - Branch logic





## Implement branch mini datapath

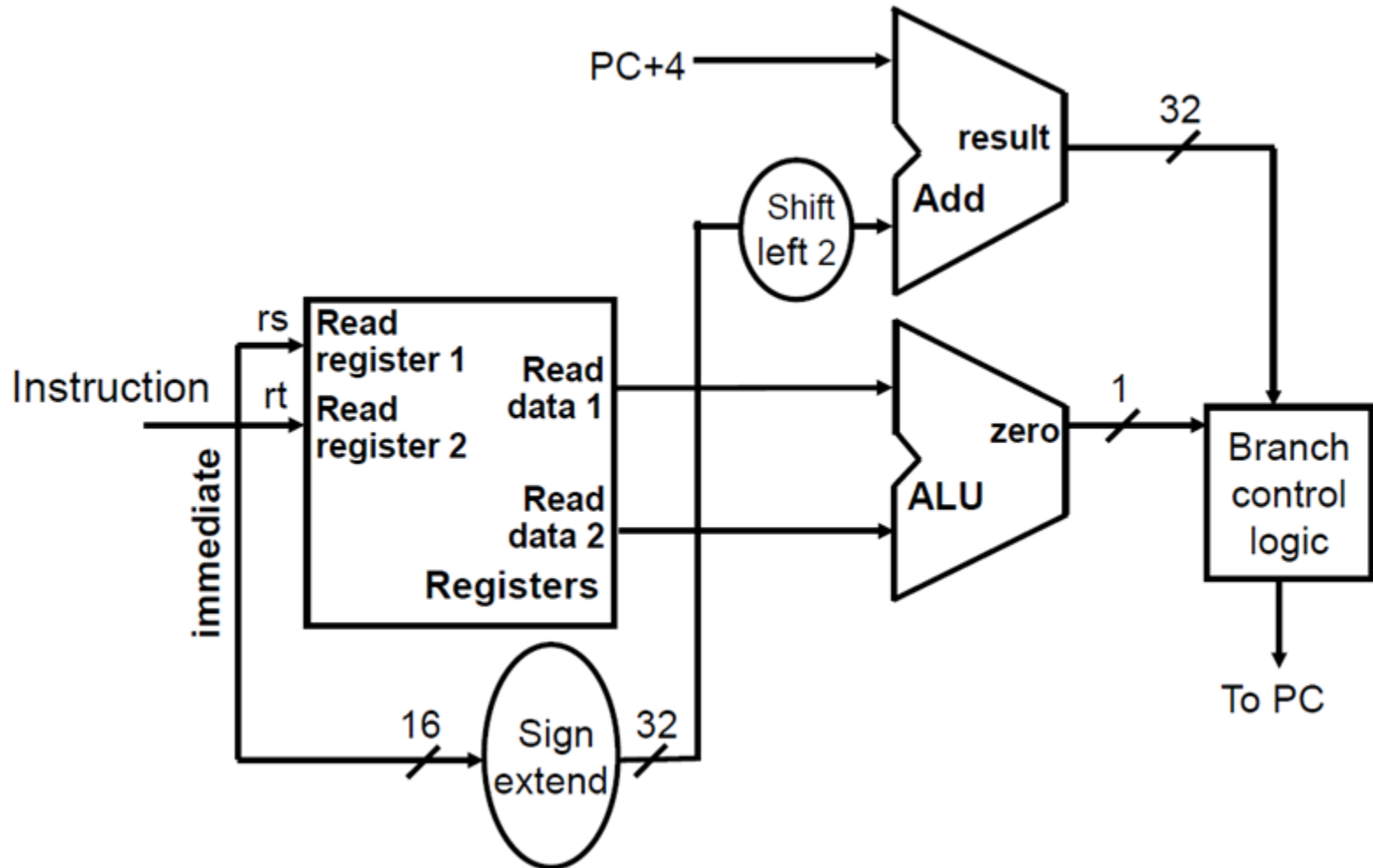


## Combine separate mini-datapaths


- Sometime sharing is possible
  - e.g. sharing of register file
- Sometime sharing is not possible
  - e.g. the branch datapath needs two ALUs
    - One for comparison operation
    - One for calculating the branch instruction address



## R-type & memory mini datapaths

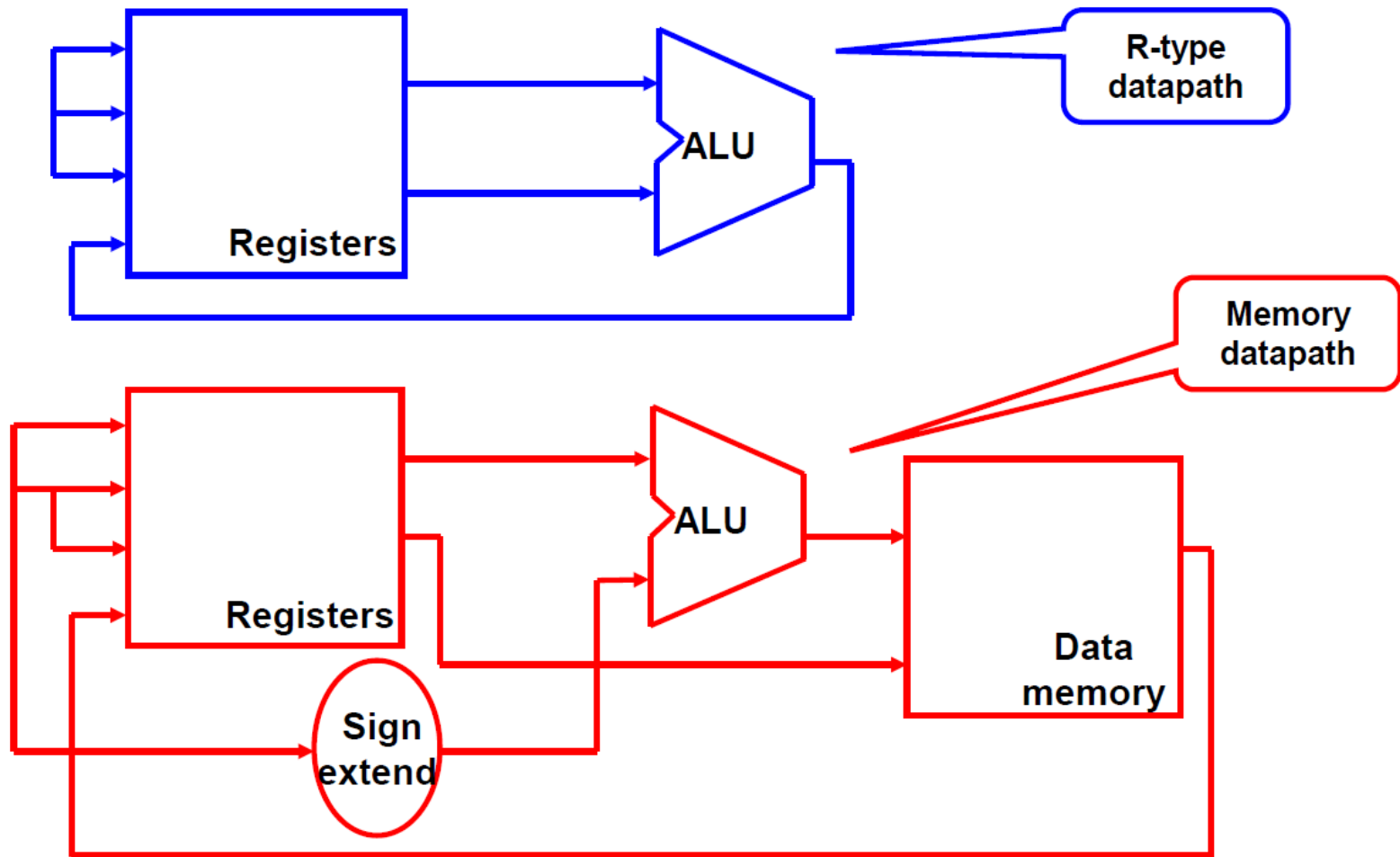


## R-type & memory datapaths combined

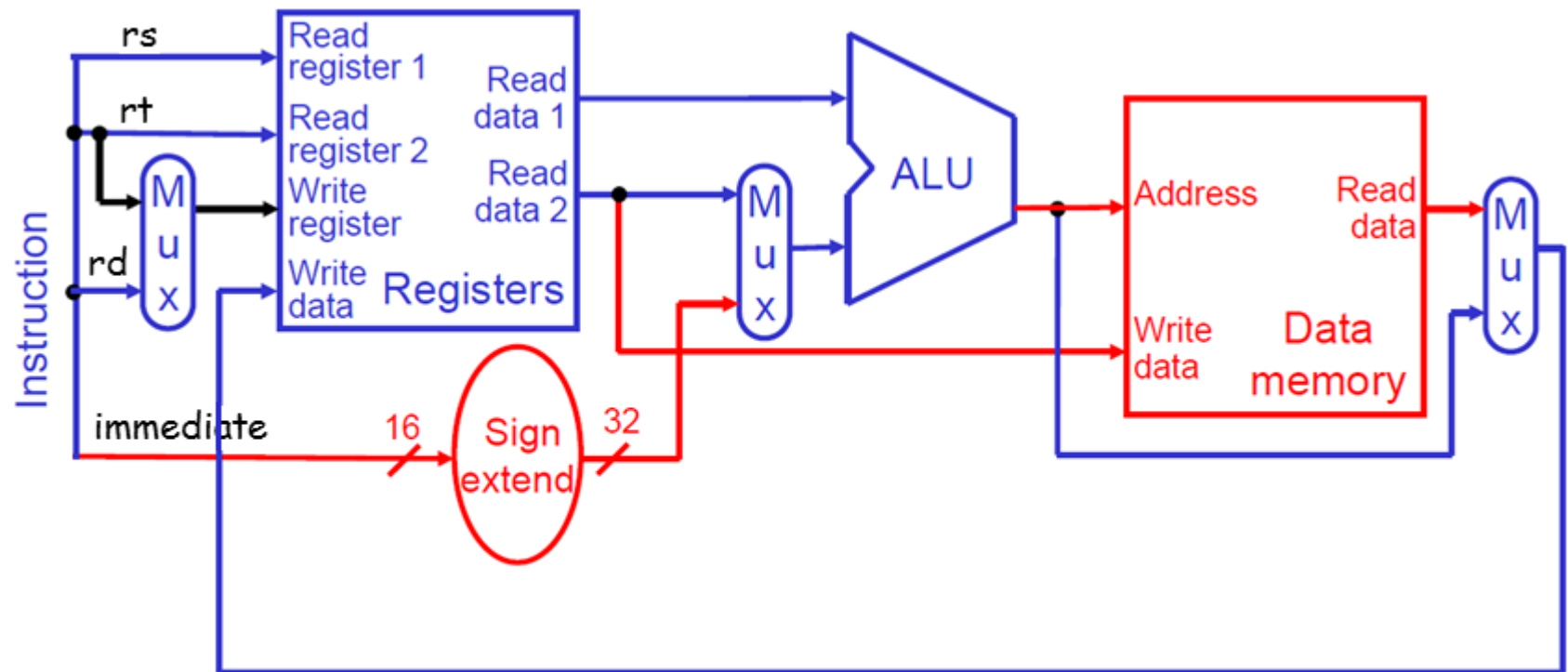

Blue – R-type Datapath

Red – what Memory Datapath adds to R-type Datapath
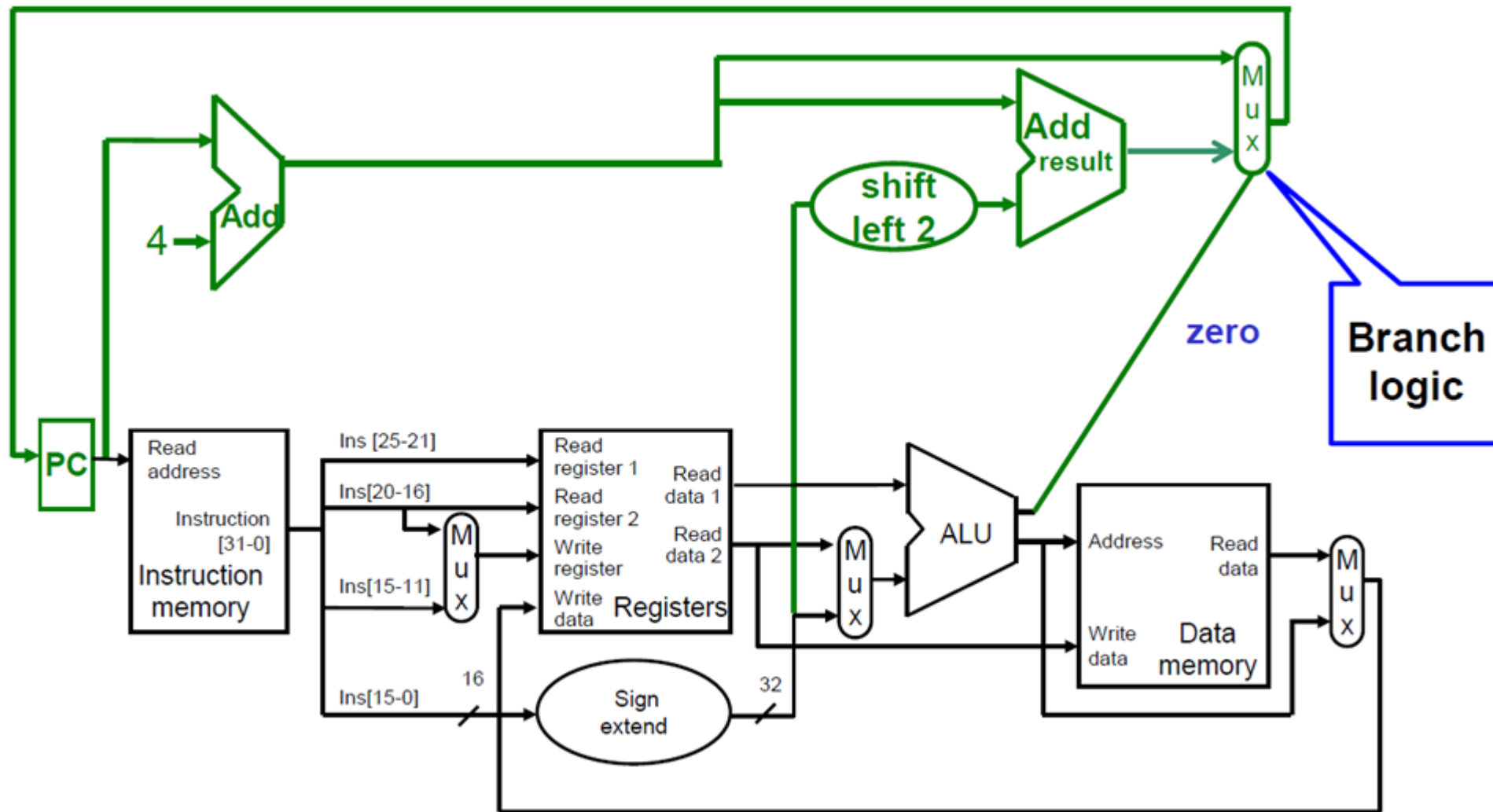
# All 3 mini datapaths & instruction fetch



## Quick exercise

- Which hardware component in the combined datapath is always used for executing every instruction?
  - A. Instruction Memory
  - B. ALU
  - C. Sign extender
  - D. None of the above

## Summary

- Instruction fetch logic
  - Fetches each 32-bit instruction
  - Updates PC
- Datapath
  - Literally, the path along which data flows
  - Connects
    - Instruction fields
    - Registers
    - ALU
    - Memory

