

NWEN 242

4. Combinational and sequential logic



Agenda



- 🕒 **Combinational logic**
 - AND gate, OR gate, NOT (inverter) gate
 - Multiplexors
 - Decoders

- 🕒 **Sequential logic**
 - S-R latch
 - D latch (S-R latch with a clock)
 - D flip-flop


- 🕒 **Register file**

Types of logic circuit

- ⌚ In digital circuit theory, **combinational logic** is a type of digital logic where the **output** is a pure function of the present **input** only.
- ⌚ **Sequential logic**, in which the output depends not only on the present input but also on the history of the input.
 - In other words, **sequential logic has memory while combinational logic does not.**

Definition of TRUE of ASSERTED

 - ⌚ Modern digital computers use **two-level logic**
- ⌚ Not all digital computers use a high voltage for binary 1 and a low voltage for binary 0
 - People talk about "**true**" or "**asserted**" and "**false**" or "**deasserted**"
 - To make things simple, we map **asserted** to **1** and **deasserted** to **0**



AND and OR gates

$$c = a \cdot b$$

Boolean
expression



Logic gate

a	b	c
0	0	0
0	1	0
1	0	0
1	1	1

Truth table

$$c = a + b$$

Boolean
expression



Logic gate

a	b	c
0	0	0
0	1	1
1	0	1
1	1	1

Truth table


Inverter gate

- ⌚ The inverter gate performs the logic operation NOT



$$c = \bar{a}$$

Boolean
expression

 




Logic gate

a	c
0	1
1	0

Truth table

"Bubbles"

   - ⌚ The NOT gate is sometimes denoted by a circle on an output or input




Quick exercise

⌚ A toggle operation cannot be performed by using a single

- A. NOT gate
- B. AND gate
- C. XOR gate
- D. None of the above

A	B	out
0	0	0
0	1	1
1	0	1
1	1	0

 



How to design a logic block using gates?

- ⌚ Goal: identify a **logic function**
- ⌚ Design steps:
 - Represent the logic function using a **truth table**
 - Each row associated with an asserted output
 - Use an **AND gate** to represent each **conjunction term**
 - Connect all inputs with an **AND gate**
 - Connect all conjunction terms through disjunction
 - Use an **OR gate** to represent each **disjunction**

Example


- ⌚ Design a logic block using gates
- ⌚ Consider a **three input** and **one output** logic function:

The output **D** is **true** when two and only two of the inputs **A**, **B**, and **C** are **true**

Truth Table			
A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0


$$D = \bar{A} \bullet B \bullet C + A \bullet \bar{B} \bullet C + A \bullet B \bullet \bar{C}$$

Answer: The logic block using gates

 

$$D = \bar{A} \bullet B \bullet C + A \bullet \bar{B} \bullet C + A \bullet B \bullet \bar{C}$$

Multiplexors

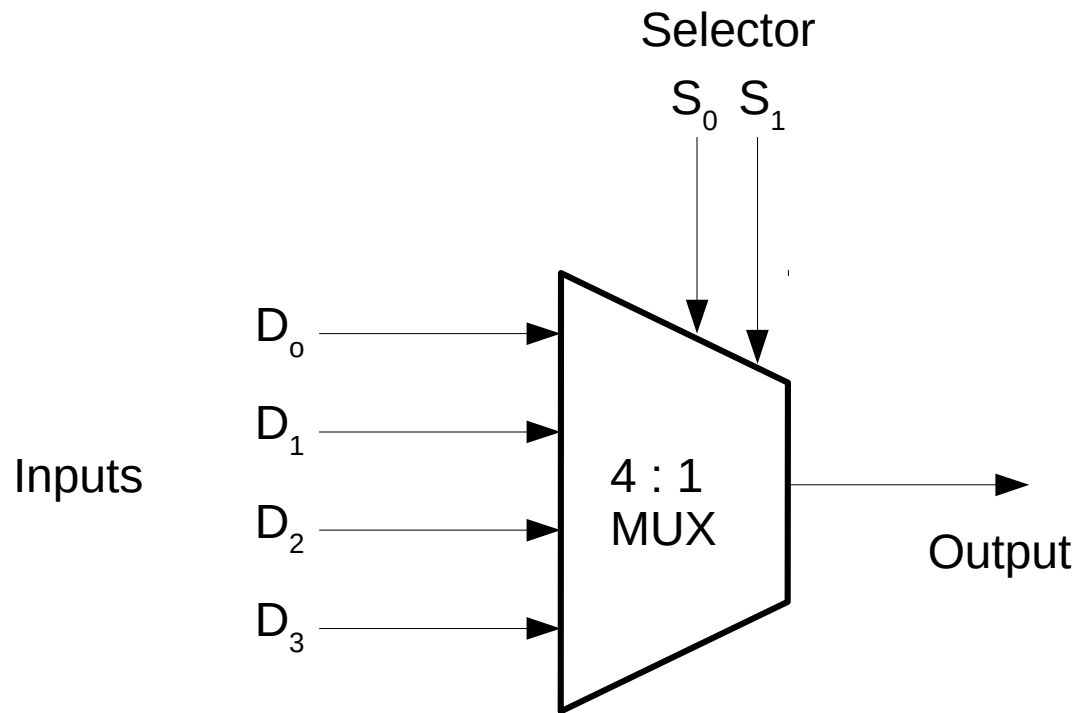

Inputs might be 1 or 2 bits or words of 32 bits
The output will be ONE of the inputs


Multiplexors

⌚ A multiplexor is a combinational logic block containing n data inputs and 1 output

⌚ The s selector inputs determine which of the n inputs will be the output.

$$s = \lceil \log_2 n \rceil$$

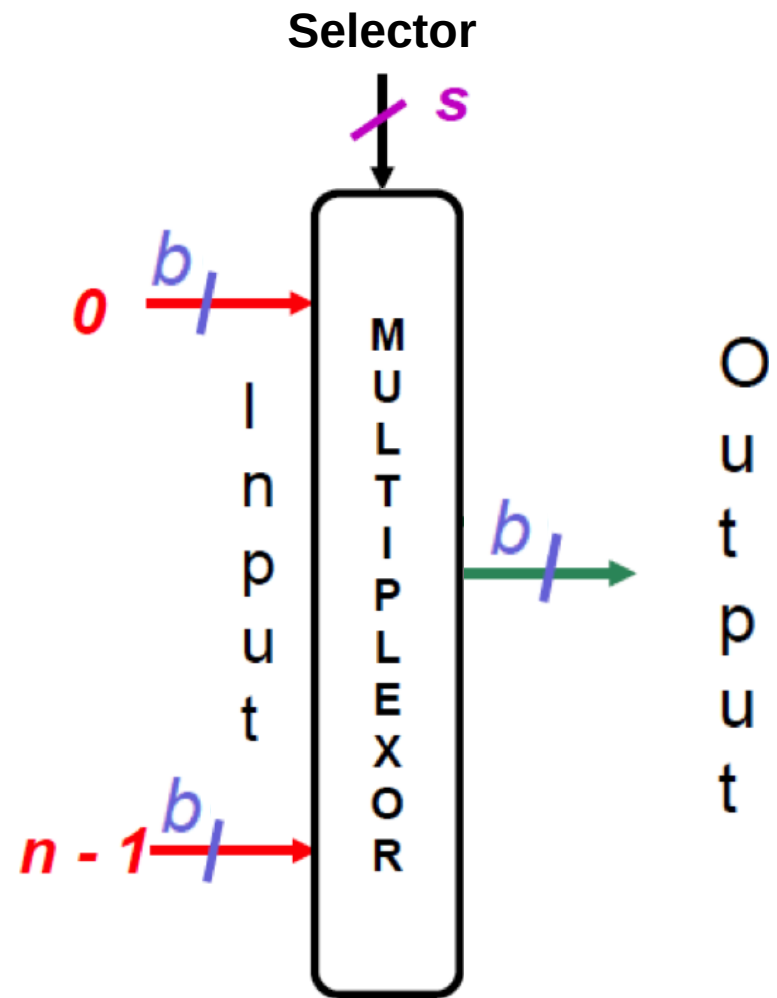⌚ If each input is a bunch of b bits, then the output is also a bunch of b bits.



Design a multiplexor



- ⌚ Let **$n = 4$ inputs**
 - then **$s = \log_2 n = \log_2 4 = 2$ bits** (S_0, S_1)
- ⌚ Let **$b = 2$ bits**, input pairs (a_0, a_1) , (b_0, b_1) , (c_0, c_1) , and (d_0, d_1)
- ⌚ Then the multiplexor's **truth table** is:

➔


Selector Inputs		Outputs	
s_0	s_1	o_0	o_1
0	0	a_0	a_1
0	1	b_0	b_1
1	0	c_0	c_1
1	1	d_0	d_1

$$S_0 = 0, S_1 = 0 \quad \text{➔} \quad O_0 = A_0, O_1 = A_1,$$

$$O_0 = \overline{S_0} \cdot \overline{S_1} \cdot A_0$$

$$O_1 = \overline{S_0} \cdot \overline{S_1} \cdot A_1$$

Multiplexor logic block

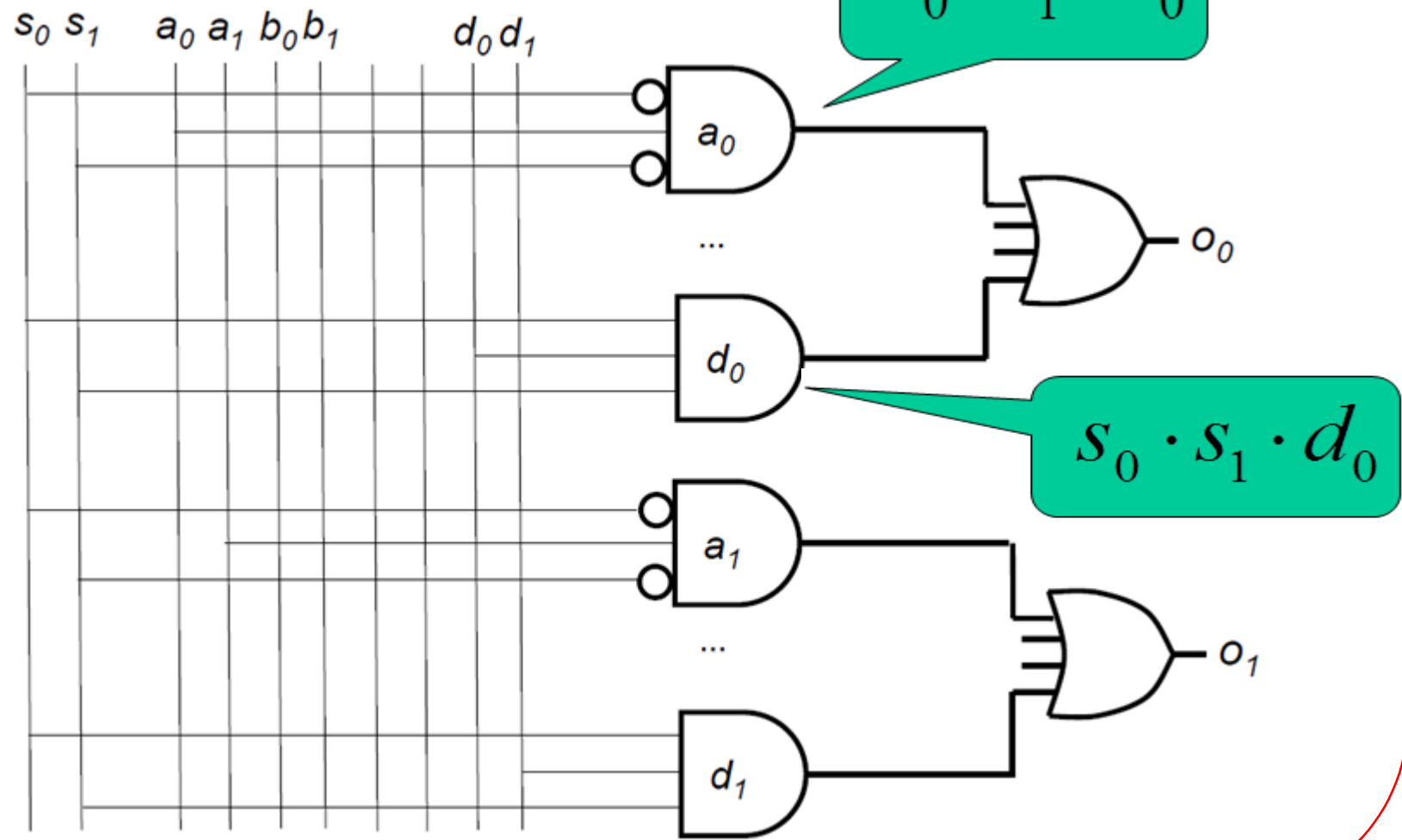

Decoders




⌚ A 3-to-8 decoder example

⌚ If we interpret the 3 inputs as a 3-bit binary number n

- Then the active output is output n

 ⌚ Generally, we talk about n -to- 2^n decoders



$$\text{In}_0 = 0$$

$$\text{In}_1 = 1$$

$$\text{In}_2 = 0$$



$$\text{Out}_0 = 0$$

$$\text{Out}_1 = 0$$

$$\text{Out}_2 = 1$$

$$\text{Out}_3 = 0$$

...


Decoder truth table

$$\overline{In_0} \cdot \overline{In_1} \cdot \overline{In_2}$$

Inputs			Outputs							
<i>In2</i>	<i>In1</i>	<i>In0</i>	<i>Out7</i>	<i>Out6</i>	<i>Out5</i>	<i>Out4</i>	<i>Out3</i>	<i>Out2</i>	<i>Out1</i>	<i>Out0</i>
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

Quick exercise

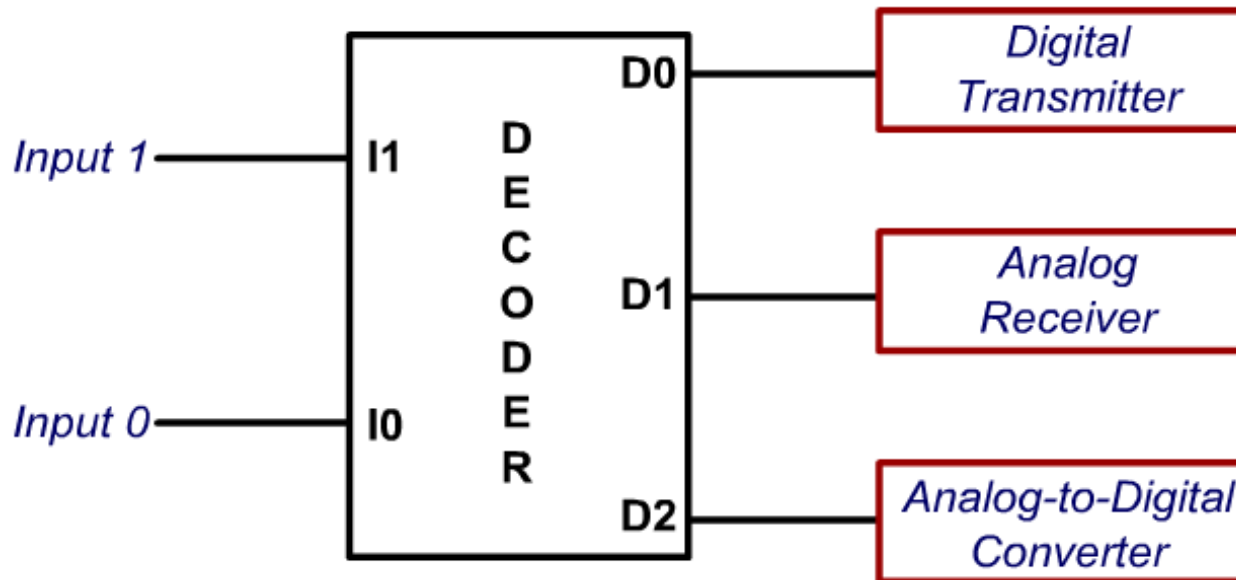- ⌚ A decoder is set up as shown, what should the input sequence be to for the Digital Transmitter?



- A: $In_1 = 0, In_0 = 1$
- B: $In_1 = 1, In_0 = 0$
- C: $In_1 = 0, In_0 = 0$
- D: $In_1 = 1, In_0 = 1$

The register




- ⌚ In MIPS, you have 32 registers
- ⌚ You can store data in registers and later read from them
- ⌚ The set of registers is called the register file
- ⌚ It is built of multiplexors, decoders, and flip-flops
- ⌚ We have discussed multiplexors and decoders
- ⌚ Next flip-flops.

Sequential logic



A clock signal

 
- ⌚ **Sequential logic** blocks usually update their output on the clock edge



- ⌚ This is **edge-triggered clocking**
- ⌚ Change in inputs at any other time have no effect on the outputs

Set-reset (SR) latch

 
- ⌚ Inputs
 - Reset
 - Set
- ⌚ Not clocked
- ⌚ Output undefined when **S and R asserted simultaneously**



NOR		
0	0	1
0	1	0
1	0	0
1	1	0


Q	S	R	Q _n
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	?
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	?

State transition table

 


Q	S	R	Q_n
0	0	0	0
0	0	1	
0	1	0	
0	1	1	?
1	0	0	
1	0	1	
1	1	0	
1	1	1	?

State
transition
table

 


Q	S	R	Q _n
0	0	0	0
0	0	1	
0	1	0	
0	1	1	?
1	0	0	1
1	0	1	
1	1	0	
1	1	1	?

State
transition
table

 

Q	S	R	Q _n
0	0	0	0
0	0	1	
0	1	0	1
0	1	1	?
1	0	0	1
1	0	1	
1	1	0	1
1	1	1	?



State
transition
table

 

Q	S	R	Q_n
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	?
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	?

State
transition
table

S-R latch example

  

At t_4
Q = Asserted
or
Q = Deasserted