 


Sequential logic



A clock signal


- ⌚ **Sequential logic** blocks usually update their output on the clock edge



- ⌚ This is **edge-triggered clocking**
- ⌚ Change in inputs at any other time have no effect on the outputs

Set-reset (SR) latch

 
- ⌚ Inputs
 - Reset
 - Set
- ⌚ Not clocked
- ⌚ Output undefined when **S** and **R** asserted simultaneously



NOR		
0	0	1
0	1	0
1	0	0
1	1	0


Q	S	R	Q _n
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	?
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	?

State transition table

 


Q	S	R	Q _n
0	0	0	0
0	0	1	
0	1	0	
0	1	1	?
1	0	0	
1	0	1	
1	1	0	
1	1	1	?

State
transition
table

 


Q	S	R	Q_n
0	0	0	0
0	0	1	
0	1	0	
0	1	1	?
1	0	0	1
1	0	1	
1	1	0	
1	1	1	?

State
transition
table

 

Q	S	R	Q _n
0	0	0	0
0	0	1	
0	1	0	1
0	1	1	?
1	0	0	1
1	0	1	
1	1	0	1
1	1	1	?



State
transition
table

 

Q	S	R	Q_n
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	?
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	?

State
transition
table

S-R latch example

 
 



At t_4
Q = Asserted
or
Q = Deasserted


D latch


⌚ D latches are **level triggered** with inputs

- C, a clock input
- D, a data input

  


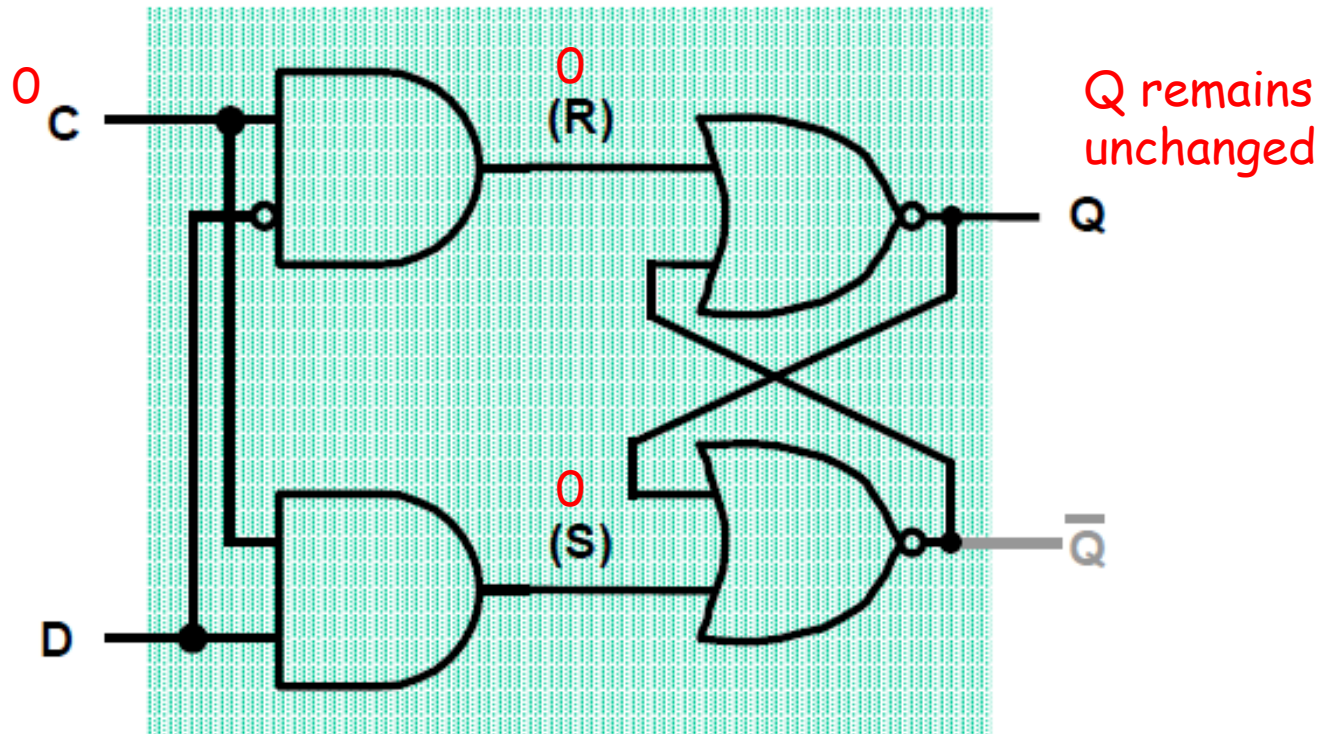

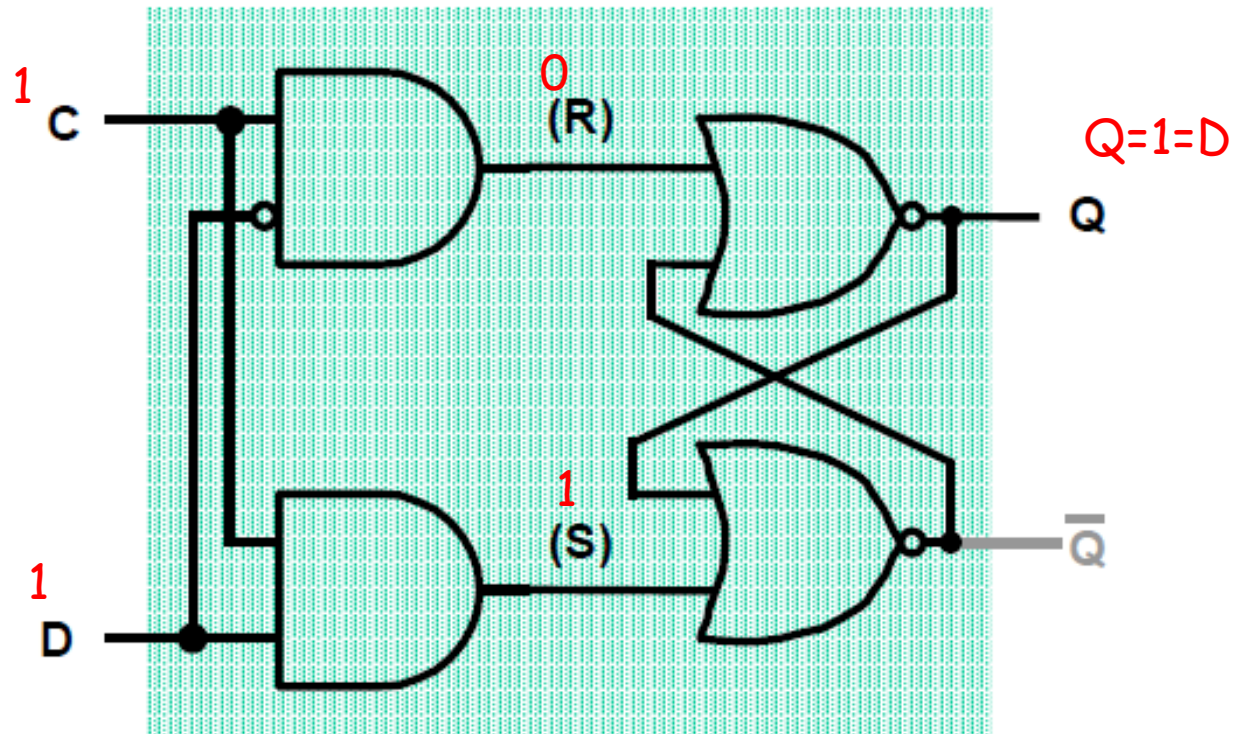

 



D latch example

 

t	C	D	S	R	Q
t_0	0	1	0	0	0
t_1	1	1	1	0	1
t_2	0	1	0	0	1
t_3	0	0	0	0	
t_4	1	0	0	1	
t_5	0	0	0	0	


D flip flops

  - ⌚ Flip-flops are **non-transparent** latches




- ⌚ When **C** is asserted, the first latch, the **master**, is open and follows the input **D**, $Q_1 = D$
- ⌚ When **C** changes to deasserted, the first latch is closed, but the second latch, the **slave**, is open: $Q_2 = Q_1$

Flip-flops example

 

t	C	$\neg C$	D	$Q1$	Q
t_0	0	1	1	0	0
t_1	1	0	1	1	0
t_2	0	1	1	1	1
t_3	1	0	0	0	1
t_4	0	1	0	0	

 

Register file


- ⌚ A **register** can be made by combining several **flip-flops**
 - e.g. 32 flip-flops to make one MIPS register
 - Each flip-flop stores one bit
 - Several registers can then be combined into a **register file**
 - Each register in the register file gets a **number n** (**address**)
- ⌚ There are two basic operations
 - **read_register**(n,d) - delivers data d from register n to ALU or memory
 - **write_register**(n,d) - inserts data d into the register number n

Register file design




The register file has:

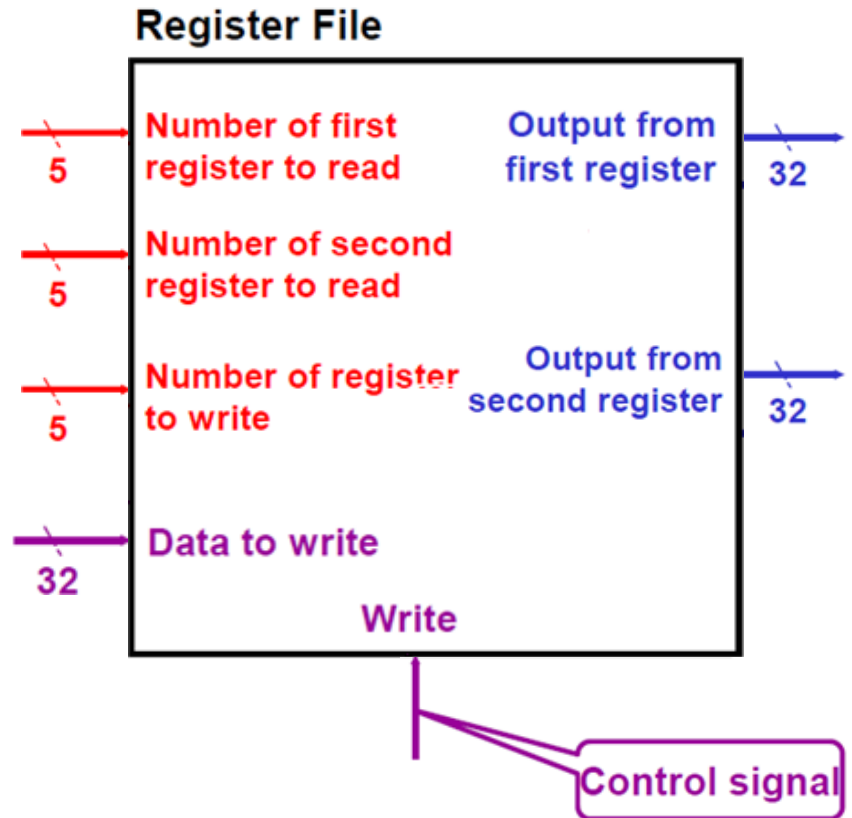- 32 registers
- Three register **address inputs**
- Two **output ports**
 - Output from source register
 - Output from target register
- One **data input** port (data to write)
- **Write control input**




Reading from the register file

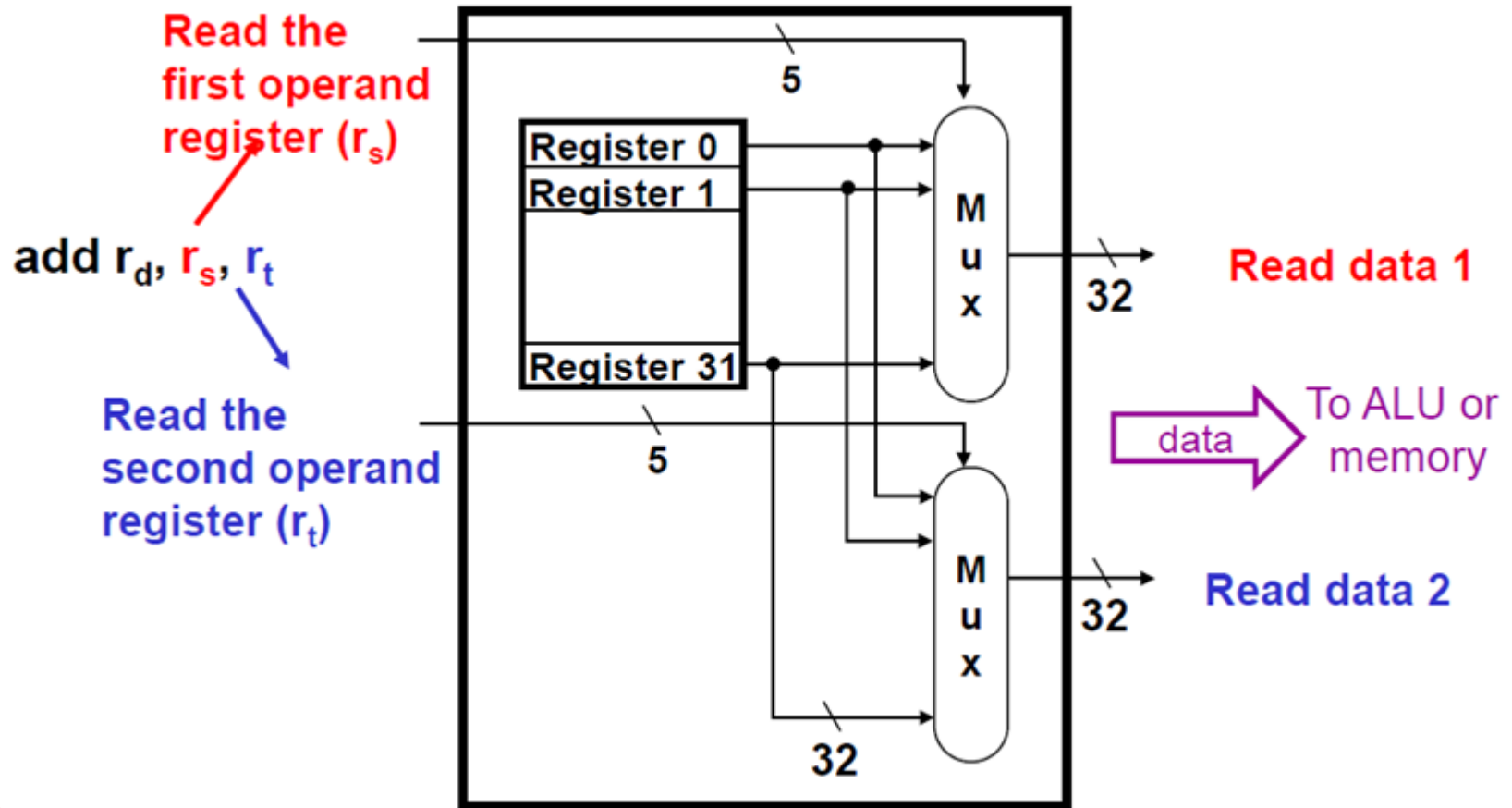

Writing to the register file

Write control signal acts as a clock

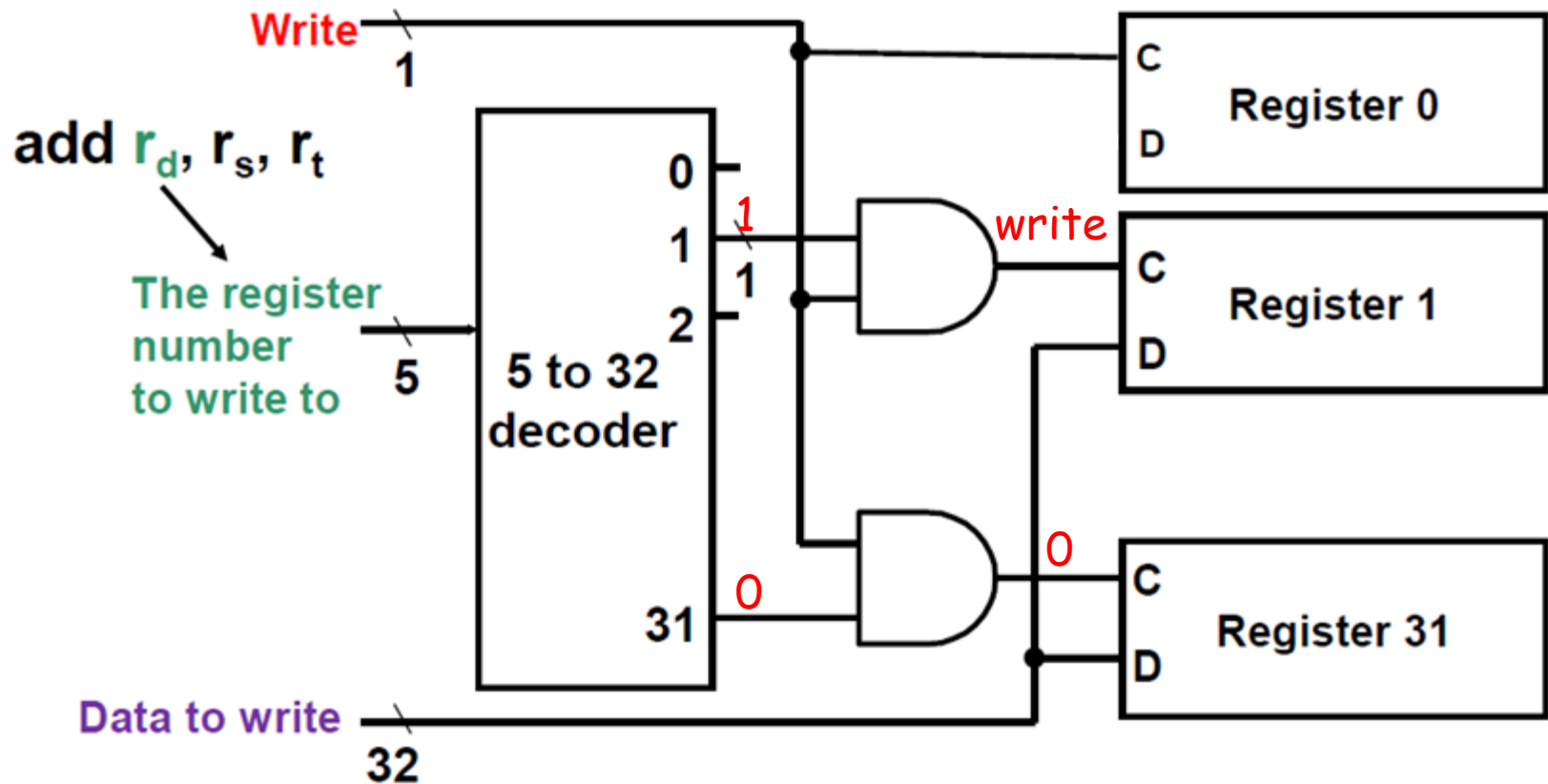

Why so few registers?



- ⌚ We need 32 flip-flops per register
- ⌚ We have $n=32$ registers
- ⌚ Each flip-flop is made up of 15 gates
 - 7 gates for a D latch + 1 for inverter
- ⌚ Total gates of the flip-flops: $32 \times 32 \times 15 = 15,360$ gates
- ⌚ And each gate needs multiple transistors

Summary



- ⌚ Combinational logic blocks are made of AND, OR, and NOT basic gates
 - The output is determined solely by inputs, it does not depend on what was before (no memory)
 - Multiplexors
 - Decoders
- ⌚ For sequential logic, the output depends not only on the present input but also on the history of the input
 - Latches and flip-flops are cross-coupled NOR gates
 - S-R latch remembers state until changed
 - D latch (advanced S-R latch)
 - Flip-flops (advanced D latch)
- ⌚ Register file
 - 32 register (each has 32 flip-flops), 2 multiplexors and 1 decoder
 - Read at most two registers at one time and write at most one.